

"FPGA-Programming" Exercise Sheet IV:

Counter

Goal of this exercise is to learn, how to describe and utilize counters with VHDL.

As target hardware always choose FPGA chip Cyclone V SoC 5CSEMA5F31C6

1) Synchronous counter with T-flip-flops

Following figure shows a synchronous 4-bit counter based on four toggle flip-flops elements.

 


Figure 1.1: Circuit of a synchronous 4-bit counter

The counter increments its value on each positive edge of the clock if the *Enable* signal is high. The counter is reset to zero on the next positive clock edge by a synchronous *low-active Clear* input.

Goal of this part is to first implement a 8-bit version of the counter. Perform following steps:

- i) Create a new Quartus project for the circuit, named **e_my_TFFcounter**.
- ii) Include the VHDL sub-level entity **e_hex7seg** of exercise sheet III).
- iii) Describe the VHDL sub-level entity of a T-flip-flop (**e_ToggleFF**).
Use a *sequential process* with synchronous low-active reset.
- iv) Create the VHDL top-level entity (**e_my_TFFcounter**) of the 8-bit synchronous T-FF counter (**a_myTFFcounter_1**). Therefore 8 instances of the toggle flip-flop component should be used. In the design use *KEY[0]* for the *Clock* input, use switch *SW[1]* for the *Enable* input and switch *SW[0]* for the *Reset* input. Furthermore use the 7-segment displays *HEX1* and *HEX0* in order to display the counter value in a hexadecimal fashion and *LEDR* to display the counter value in a binary fashion.
- v) Import the necessary pin assignments and compile the circuit. From the **Compilation Report** learn the number of resulting logic elements. Perform a functional simulation by creating a **test bench** and verify the correct functionality.
- vi) Download the counter circuit to the FPGA device and test the functionality.
- vii) Also implement a 4-bit version (**a_myTFFcounter_2**) of the circuit and use the **RTL Viewer** to examine how Quartus synthesises the circuit. What are the differences in comparison with above figure?

2) Synchronous counter using high-level statements

Another way to specify a counter is by using a register (by using a **std_logic_vector** signal) and cyclically adding 1 to its value.

This can be accomplished using the following VHDL statement:

```
Q <= Q + 1;
```

Goal of this part is to first implement a 16-bit version of the synchronous counter by using the syntax stated above. Perform following steps:

- i) Create a new Quartus project for the circuit, named **e_my_counter**.
- ii) Include the VHDL sub-level entity **e_hex7seg** of part 1).
- iii) Create a VHDL top-level entity (**e_my_counter**) for the 16-bit synchronous counter. Include all functions of **std_logic_unsigned** from the **ieee** library and describe the architecture of the circuit named **a_my_counter_1** with high-level syntax.

Use *KEY*[0] as *Clock* input, switch *SW*[1] as *Enable* input and switch *SW*[0] as synchronous *Reset* input. Use the four 7-segment displays *HEX3* to *HEX0* to display the counter value in a hexadecimal fashion.
- iv) Import the necessary pin assignments and compile the circuit. From the **Compilation Report** learn the number of resulting logic elements. Perform a functional simulation by creating a **test bench** and verify the correct functionality.
- v) Download the counter circuit to the FPGA device and test the functionality.
- vi) Also implement a 4-bit version (**a_mycounter_2**) of the circuit and use the **RTL Viewer** to examine how Quartus synthesises the circuit. What are the differences compared to the design of part 1) ?

3) *Synchronous counter using a LPM module*

Another way to describe a synchronous counter is by using a LPM module, which should be demonstrated within the part. A tutorial for using LPM modules in Quartus 17.0 can be found following the link:

ftp://ftp.altera.com/up/pub/Intel_Material/17.0/Tutorials/VHDL/Using_Library_Modules.pdf

For the realisation of the counter using a LPM module perform following steps:

- i) Create a new Quartus project for the circuit, named **e_my_LPMcounter**. As LPM module use **lpm_counter** for the implementation of the 16-bit counter. Name the LPM module **e_lpm_count**.
- ii) Parametrize the LPM module in a way to exhibit a *enable* input and a synchronous *reset (clear)* input.
- iii) In the design use push-button *KEY*[0] as *Clock* input, switch *SW*[1] as *Enable* input and switch *SW*[0] as synchronous *Reset* input. Furthermore use the four 7-segment displays *HEX3* to *HEX0* in order to display the counter value in a hexadecimal fashion.
- iv) Import the necessary pin assignments and compile the circuit. From the **Compilation Report** learn the number of resulting logic elements. Perform a functional simulation by creating a **test bench** and verify the correct functionality.
- v) Download the counter circuit to the FPGA device and test the functionality.

4) Running digits

Goal of this part is to design a circuit that successively flashes the digits 0 through 9 on the 7-segment display *HEX0*. Each digit should be displayed for about one second. Use a counter to determine the approximately one-second intervals. As clock input signal of the counter the 50 MHz clock signal of the development board (**CLOCK_50**) must be used. No other clock signals should be derived in the design. All flip-flops of the design should be clocked directly by the same 50 MHz clock signal.

Following figure shows a small part of the design which should be created. The figure illustrates how a large bit-width counter can be used to produce an *enable* signal for a smaller counter. The rate at which the smaller counter increments can be controlled by choosing an appropriate number of bits in the larger counter.

 


Figure 4.1: Possibility for the realisation of a slow counter

Implement and test this circuit. Perform following steps:

- i) Create a new Quartus project for the circuit, named **e_my_slowclock**.
- ii) Create a VHDL sub-level entity (**e_bcd7seg**), which uses a *combinatorial process* named **p_decode** that decodes a 4-bit vector as BCD number for driving a 7-segment display.
- iii) Describe the functionality (**a_my_slowclock_1**) within the VHDL top-level entity. For both, the implementation of the fast (**p_slow_clock**) and the slow (**p_4bit_cnt**) counter use a *sequential process*. Determine the minimal bit-width of the counter value of the fast counter in order to display each number for round about one second.
- iv) Import the necessary pin assignments, compile and download the circuit and test its functionality.
- v) Furthermore create a second architecture description (**a_my_slowclock_2**) in which the behaviour will be described in a way that each number will be shown **exactly** for one second. Furthermore add a synchronous low-active reset (**KEY[0]**) to both counter and modify the enable condition in a way that the number 0 after reset will also be displayed for one second. Compile, download and test the circuit again.

5) Rotating word

Within this part the word **dE1** should rotate on the three 7-segment displays *HEX2* to *HEX0* from right to left in one-second intervals. Following table clarifies the rotation:

Clock cycle	Display
0	d E 1
1	E 1 d
2	1 d E

Different possibilities for the realisation exist. One possibility is to re-use the VHDL code of exercise sheet I) part 5). Only small changes are necessary by replacing both switches by a 2-bit wide counter, which will be incremented at one-second intervals.

For the description of the circuit, perform following steps:

- i) Create a new Quartus project for the circuit, named **e_my_rotatingDE1**.
- ii) Use the description of the fast counter of part 4) to provide an *enable* signal of precisely one-second interval. Implement a slow 2-bit wide counter (**p_2bit_cnt**) which only uses three of the four possible states. Use push-button *KEY*[0] as synchronous reset for both counter.
- iii) Include the VHDL entities **e_char7seg** and **e_2bit3to1mux** from exercise sheet I) part 5).
- iv) Import the necessary pin assignments.
- v) Compile, download and test the functionality of the circuit.

6) *Running word*

Create an extended version of the circuit of part 5) in a way that the word **dE1** runs through all six 7-segment displays from right to left. Following table illustrates the pattern:

Clock cycle	Display
0	d E 1
1	d E 1
2	d E 1
3	d E 1
4	E 1 d
5	1 d E

Perform following steps:

- i) Create a new Quartus project for the circuit, named **e_my_runningDE1**.
- ii) Describe the behaviour (**a_my_runningDE1_1**). Use the circuit of the previous part as basis and extend the functionality accordingly. Use the entities **e_char7seg** and **e_2bit6to1mux** of exercise sheet I) part 6). Use push-button $KEY[0]$ as synchronous reset for both counters.
- iii) Import the necessary pin assignments. Compile, download and test the functionality of the circuit.
- iv) Also create a further architecture description (**a_my_runningDE1_2**) which extends the functionality of the circuit by a direction signal. Use switch $SW[0]$ for the determination of the direction. If switch $SW[0] = 0$ than the pattern of the table above should be the case. If switch $SW[0] = 1$ than the direction should be the opposite. Hint: Perform the required changes in the slow counter **p_2bit_cnt**.
- v) Compile, download and test the functionality of the circuit with direction selection extension.