

## "FPGA-Programming" Exercise Sheet III:


### Latches, FlipFlops und Register

The integrated logic block of FPGA devices include flip-flops, which can be utilized for the description of sequential logic and storage circuits. Goal of this exercise is to examine latches, flip-flops and registers.

**As target hardware always choose FPGA chip Cyclone V SoC 5CSEMA5F31C6**

#### 1) Gated RS-latch


Within this part, it should be demonstrated how storage elements can be described in FPGA devices, without using dedicated flip-flops of the chip. Following figure illustrates a *gated RS-latch*.

 

**Figure 1.1:** Circuit of a gated RS-latch


- i) From the given circuit, derive the complete truth table and describe the logic functions for outputs  $Q$  and  $\bar{Q}$ .

If this gated RS-latch should be implemented inside of a FPGA chip, which contains Lookup Tables (LUTs) with 4 inputs, then only one LUT block will be needed in order to realize the functionality as following figure shows.

 

**Figure 1.2:** Implementation of a gated RS-latch in a single LUT

Although a gated RS-latch can be implemented in a single LUT, this implementation does not allow to observe the internal signals  $R_g$  and  $S_g$ . The internal signals will be cleaned out by the compiler for optimization. If the signals must be observed, for instance during simulation, a so called *compiler assignment* must be used, which instructs Quartus to use discrete LUTs for the implementation of the signals  $R_g$ ,  $S_g$ ,  $Q$  and  $\bar{Q}$ . Following figure illustrates the LUT implementation when using the compiler assignment **keep** by a VHDL **attribute** statement.

 


**Figure 1.3:** Implementation of a gated RS-latch in four discrete LUTs

Implement the circuit of the gated RS-latch. Perform following steps:

- ii) Create a new Quartus project for the circuit, named **e\_my\_gatedRSlatch**.
- iii) Describe the architecture (**a\_my\_gatedRSlatch\_1**) for the circuit of the gated RS-latch using boolean expressions **without** using the **keep** attribute. Compile the circuit and analyse it with Quartus **RTL Viewer** and **Technology Map Viewer**.
- iv) Add an additional architecture description (**a\_my\_gatedRSlatch\_2**) in which the **keep** attribute for the internal signals  $R_g$ ,  $S_g$ ,  $Q$  and  $\bar{Q}$  is used. Describe a configuration block named **c\_my\_gatedRSlatch** and configure it to use the second architecture description. Compile the circuit and analyse it using Quartus **RTL Viewer** and **Technology Map Viewer**.

## 2) Gated D-latch

Following figure shows the circuit of a gated D-latch which should be examined similar to the one of part 1).

 


**Figure 2.1:** Circuit of a gated D-latch

Perform following steps:

- i) From the given circuit, derive the complete truth table and describe the logic function for the outputs  $Q$  and  $\bar{Q}$ .
- ii) Create a new Quartus project for the circuit, named **e\_my\_gatedDlatch**.
- iii) Create a VHDL sub-level entity named **e\_gatedDlatch**. Describe the architecture of the gated D-latch using boolean expressions both **without** using the **keep** attribute (**a\_gatedDlatch\_1**) and **with** using the **keep** attribute (**a\_gatedDlatch\_2**).
- iv) Create the VHDL top-level entity named **e\_my\_gatedDlatch** in which the component **e\_gatedDlatch** will be instantiated. Use the **configuration specification** syntax to first include the instance named **I\_DLatch** using the architecture description without the keep attribute set (**a\_gatedDlatch\_1**). Compile the circuit and analyse it with Quartus **RTL Viewer** and **Technology Map Viewer**.
- v) Configure the circuit to use architecture description **a\_gatedDlatch\_2** for the instance **I\_DLatch**. Compile the circuit and analyse it with Quartus **RTL Viewer** and **Technology Map Viewer**.
- vi) For input  $D$  use switch  $SW[0]$ , for input  $Clk$  use switch  $SW[1]$ . Output  $Q$  should be assigned to  $LEDR[0]$ . Import the necessary pin assignments, compile the circuit and download the compiled circuit into the FPGA.
- vi) Test the functionality of the circuit in hardware.

### 3) Gated Master-Slave D-latch

Following figure shows the circuit of a *gated MS-D-latch*, which should be analysed in this part.

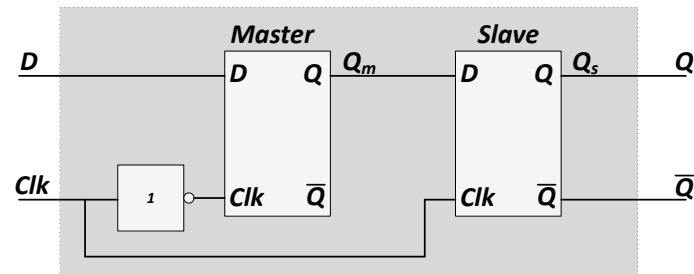


**Figure 3.1:** Circuit of a gated Master-Slave D-latch

Perform following steps:

- i) Create a new Quartus project for the circuit, named **e\_my\_gatedMSDlatch**. Create a VHDL top-level entity which includes two instances (**I\_MDLatch** and **I\_SDLatch**) of the gated D-latch (**e\_gatedDlatch**) from part 2). The two instances should be configured to use the architecture description which does not use the **keep** attribute (**a\_gatedDlatch\_1**).
- ii) For input *D* use switch *SW*[0], for the input *Clk* use switch *SW*[1]. Output *Q* should be assigned to *LEDR*[0]. Furthermore the Output of the Master *Q<sub>m</sub>* should be assigned to *LEDR*[1]. Import the necessary pin assignments and compile the circuit.
- iii) Analyse the circuit with Quartus **Technology Map Viewer**.
- iv) Download the circuit and test the functionality in hardware.


#### 4) Comparison of different D-type flip-flops

Following figure shows a circuit, consisting of three different storage elements, one gated D-latch, as well as a positive-edge triggered D-flip-flop and a negative-edge triggered D-flip-flop.

 

**Figure 4.1:** Three different D-flip-flop types

Following timing diagram clarifies the behaviour of the individual flip-flops.

 

**Figure 4.2:** Timing diagram for the three types of D-flip-flop

Implement and simulate this circuit. Perform following steps:

- i) Create a new Quartus project for the circuit, named **e\_my\_DtypeFFs**.
  - ii) Write a VHDL sub-level entity (**e\_gatedDlatch**) for the description of a gated D-latch **without** usage of the **keep** attribute.  
Describe the behaviour by using a combinatorial process.
  - iii) Write a VHDL sub-level entity (**e\_posedgeDFF**) for the description of a positive-edge triggered D-flip-flop. Describe the behaviour by using a sequential process.
  - iv) Write a VHDL sub-level entity (**e\_negedgeDFF**) for the description of a negative-edge triggered D-flip-flop. Describe the behaviour by using a sequential process.
  - v) Create a top-level entity (**e\_my\_DtypeFFs**) which includes all three components. Compile the circuit.
  - vi) By using the Quartus **Technology Map Viewer** verify that the gated D-latch will be implemented in one single LUT, whereas the positive-edge triggered D-flip-flop and negative-edge triggered D-flip-flop will be implemented in discrete flip-flop blocks of the target FPGA.
  - vii) Perform a functional simulation with ModelSim and examine the behaviour of the three D-type flip-flops.
-

### 5) Simple example to storage elements

Within this part the hexadecimal value of a 8-bit number  $A$  should be displayed on the 7-segment displays  $HEX3$  and  $HEX2$ . Furthermore the hexadecimal value of a 8-bit number  $B$  should be displayed on the 7-segment display  $HEX1$  and  $HEX0$ . The values of  $A$  and  $B$  are the inputs of the circuit which will both be provided by the switches  $SW[7 - 0]$ .

To input the values of  $A$  and  $B$ , first the value for  $A$  should be set by the switches and stored in a register, before the value of  $B$  will be set by the very same switches.

Furthermore an adder circuit should be described, which calculates the arithmetic sum  $S = A + B$ , and displays this sum on the 7-segment display  $HEX5$  and  $HEX4$ . The carry output produced by the adder should be shown on  $LEDR[0]$ .

Perform following steps:

- i) Create a new Quartus project for the circuit, named **e\_my\_reg**.
- ii) Create a VHDL sub-level entity named **e\_hex7seg**. Describe a 7-segment decoder which interprets a 4-bit input vector as hexadecimal number and decodes it for displaying it on a 7-segment display. Use a combinatorial process named **p\_Decode** together with a **case** statement.
- iii) Create a VHDL sub-level entity named **e\_reg\_arn**. Describe a 8-bit wide register with *low-active asynchronous* reset. Use a sequential process.
- iv) Write the VHDL top-level entity (**e\_my\_reg**) which implements the requested functional range. Use  $KEY[0]$  as *low-active* reset and  $KEY[1]$  as manual clock input.
- v) Import the necessary pin assignments and compile the circuit.
- vi) Perform a functional simulation with ModelSim and examine the behaviour of the circuit.
- vii) Download the compiled circuit and test the functionality in hardware.