

## "FPGA-Programming" Exercise Sheet I:

### Switches, LEDs and Multiplexers

The purpose of this exercise is to learn how to connect simple input and output devices to an FPGA chip and implement a circuit that uses these devices. We will use the switches  $SW[9] - SW[0]$  on the DE1-SoC board as inputs to the circuit. We will use the LEDs and 7-segment displays as output devices.

**As target hardware always choose FPGA chip Cyclone V SoC 5CSEMA5F31C6**

#### 1) Simple switch to LED assignment

The DE1-SoC board features following switches and LEDs:


Number of Switches	Name of Switches	Number of LEDs	Name of LEDs
10	$SW[9] - SW[0]$	10	$LEDR[9] - LEDR[0]$

Write a simple VHDL program which assigns the 10 switches to the 10 red LEDs, in a way that switch  $SW[0]$  is assigned to  $LEDR[0]$ , switch  $SW[1]$  to  $LEDR[1]$  and so on. Perform following steps:

- i) Generate a new Quartus project for the circuit, named **e\_my\_first\_fpga**. Create a new VHDL file, named **e\_my\_first\_fpga.vhd**.
- ii) Create a VHDL entity and describe the architecture of the circuit, named **a\_my\_first\_fpga\_1**.
- iii) Perform an analysis and synthesis step by heading to *Processing -> Start -> Start Analysis & Synthesis* or by pressing the appropriate button.
- iv) Goto *Assignments -> Pin Planner* or press the appropriate button. In the Pin Planner assign the necessary pins. Information to perform the correct assignments can be found in the document DE1-SoC\_User\_manual.pdf provided on iLearn.
- v) Compile the circuit (*Processing -> Start Compilation*). Analyze it with Quartus **RTL Viewer** (*Tools -> Netlist Viewers -> RTL Viewer*), and **Chip Planner** (*Tools -> Chip Planner*) in order to become familiar with these tools.
- vi) Download the compiled circuit (*Tools -> Programmer or appropriate button press*) and test the functionality. Information about how to program the device can be found in the document DE1-SoC\_User\_manual.pdf under section *Configure the FPGA in JTAG Mode* starting at page 14.
- vii) Change the functionality of the circuit such that the switches will be assigned to the LEDs in reversed order, so  $SW[9]$  to  $LEDR[0]$ ,  $SW[8]$  to  $LEDR[1]$ , and so on. Use a second architecture description named **a\_my\_first\_fpga\_2** and the VHDL syntax of a **configuration** block named **c\_my\_first\_fpga**. Compile the circuit, analyze it, download it and test the functionality. Also try using internal signals.

2) *Four bit wide 2-to-1 multiplexer*

Following figure shows a simple circuit, which implements a 2-to-1 multiplexer with address input  $s$ . If  $s = 0$  then the output  $m$  will take the value of input  $x$ , otherwise the output  $m$  will take the value of input  $y$ .

 


**Figure 2.1:** Circuit of a 2-to-1 multiplexer

Based on this circuit, following abstract truth table results:

s	m
0	x
1	y


Following figure illustrates the symbol of the circuit:

 

**Figure 2.2:** Symbol of a 2-to-1 multiplexer


- i) Derive the complete truth table for the given circuit and describe the logic function for output  $m$ .

In the following a VHDL entity should be generated, which describes the circuit illustrated in the figure below.

 

**Figure 2.3:** Circuit of a 4-bit wide 2-to-1 multiplexer

The circuit has two 4-bit wide inputs  $X$  and  $Y$  and produces a 4-bit wide output  $M$ . If the address input  $s = 0$  then  $M = X$ , otherwise  $M = Y$ . The symbol of the 4-bit wide 2-to-1 multiplexer is given below:

 

**Figure 2.4:** Symbol of a 4-bit wide 2-to-1 multiplexer


Perform following steps:

- ii) Generate a new Quartus project for the circuit, named **e\_my\_4bit2to1mux**.
- iii) Create a VHDL entity and describe the circuit. Use switch  $SW[9]$  as address input  $s$ , switches  $SW[3 - 0]$  as input vector  $X$ , switches  $SW[7 - 4]$  as input vector  $Y$ . Furthermore the value of address input  $s$  should be displayed on  $LEDR[9]$ , the output vector  $M$  should be displayed on  $LEDR[3 - 0]$ . Unused LEDs should be assigned with a constant value of 0.
- iv) Import the necessary pin assignments.
- v) Compile the project, download the compiled circuit and test the functionality.

Furthermore inspect the circuit with **RTL Viewer** and **Chip Planner**.

### 3) Two bit wide 3-to-1 multiplexer

One part of previous task was the description of a 2-to-1 multiplexer. Following figure shows, how this circuit can be used for the description of a 3-to-1 multiplexer. A 3-to-1 multiplexer has three data inputs  $u$ ,  $v$  and  $w$ , which means that a two bit wide address signal  $s_1 s_0$  is needed.

 


**Figure 3.1:** Circuit of a 3-to-1 multiplexer

Based on this circuit, following abstract truth table results:

$s_1$	$s_0$	$m$
0	0	$u$
0	1	$v$
1	0	$w$
1	1	$w$


Following figure illustrates the symbol of the circuit:

 

**Figure 3.2:** Symbol of a 3-to-1 multiplexer

- Derive the complete truth table for the given circuit and describe the logic function for output  $m$ .

In the following a VHDL entity should be generated, which describes the circuit illustrated in the figure below.

 

**Figure 3.3:** Symbol of a 2-bit wide 3-to-1 multiplexer


The circuit has three 2-bit wide inputs  $U$ ,  $V$  and  $W$  and produces a 2-bit wide output  $M$ . Perform following steps:

- ii) Generate a new Quartus project for the circuit, named **e\_my\_2bit3to1mux**.
- iii) Create a VHDL entity and describe the circuit. Use switches  $SW[9 - 8]$  as address input  $s$ , switches  $SW[5 - 0]$  for the input vectors of  $U$ ,  $V$  and  $W$ . The output vector  $M$  should be displayed on  $LEDR[1 - 0]$ . Unused LEDs should be assigned with a constant value of 0.
- iv) Import the necessary pin assignments.
- v) Compile the project, download the compiled circuit and test the functionality.

Furthermore inspect the circuit with **RTL Viewer** and **Chip Planner**.

#### 4) Simple 7-segment decoder

Goal of this task is the description of a simple 7-segment decoder. The character to display depends on a 2-bit input vector. The decoder produces 7 output signals, which are used to show a character on a 7-segment display. Following figure clarifies the circuit to be described with the inputs  $c_1$   $c_0$ .

 

**Figure 4.1:** Simple 2-input 7-segment decoder

The table below states the characters, which should be displayed for different choices of  $c_1$  and  $c_0$ , including a *blank* character:

$c_1$	$c_0$	character
0	0	d
0	1	E
1	0	1
1	1	

- i) Derive the truth table for each of the individual segment of the 7-segment display and describe the logic function for each segment.

The seven segments of the display will be identified by the indices 0 up to 6. The individual segments are **low-active**, which means that a segment is illuminated if it will be driven by a logic 0. In the following a VHDL entity should be described, which implements the derived logic functions. Only use simple VHDL assignments based on Boolean expressions here. Perform following steps:

- ii) Generate a new Quartus project for the circuit named **e\_my\_7segdec**.
- iii) Create a VHDL entity for the 7-segment decoder. Connect the inputs  $c_1$   $c_0$  with the switches  $SW[1 - 0]$ , and the outputs of the decoder with the 7-segment display  $HEX0$ . The individual segments of the display are named  $HEX0[0]$  to  $HEX0[6]$ . Use following port description:


```
HEX0: out std_logic_vector (0 to 6);
```

- iv) Import the necessary pin assignments.
- v) Compile the project, download the compiled circuit and test the functionality.

Furthermore inspect the circuit with **RTL Viewer** and **Chip Planner**.

### 5) Multiplexers and 7-segment displays

Consider the circuit of following figure:

 

**Figure 5.1:** Simple controlled 7-segment decoder

The circuit uses a 2-bit wide 3-to-1 multiplexer in order to enable the selection of three characters, which should be displayed on the 7-segment display. The 7-segment decoder of part 4) permits displaying the characters *d*, *E*, 1 as well as the *blank* character.

The cipher codes should be set with switches  $SW[9 - 8]$  as given in the table below. This simple circuit can be quickly generated using the descriptions of part 3) and part 4).

$SW[9]$	$SW[8]$	character
0	0	d
0	1	E
1	0	1

Goal of this task is to describe a circuit, which enables to drive a total of three 7-segment displays instead only one. It should be utilized to *rotate* the word *dE1* in a circular fashion, as given in the table below:

$SW[9]$	$SW[8]$	$HEX2$	$HEX1$	$HEX0$
0	0	d	E	1
0	1	E	1	d
1	0	1	d	E

For the realization, three instances of the sub-level entities (**e\_2bit3to1mux** and **e\_7segdec**) will be needed, which have to be declared as **component** in the top-level entity and instantiated. Perform the following steps:

- i) Generate a new Quartus project for the circuit, named **e\_my\_mux7seg**.
- ii) Create a VHDL top-level entity for the circuit. Connect the switches  $SW[9 - 8]$  with the address inputs of the three instances of the 2-bit wide 3-to-1 multiplexer. Furthermore connect the switches  $SW[5 - 0]$  with the inputs of the three 7-segment decoder in a way to achieve the desired functionality. Show the position of the switches on the LEDs and connect the outputs of the three instances of the 7-segment decoder with the 7-segment displays *HEX2*, *HEX1* and *HEX0*.
- iii) Import the necessary pin assignments.
- iv) Compile the project, download the compiled circuit and test the functionality.  
Furthermore inspect the circuit with **RTL Viewer** and **Chip Planner**.



### 6) Rotating letters

Goal of this task is to extend the circuit of part 5) in a way that all six 7-segment displays will be driven. The circuit must be capable of displaying the word *dE1* on three 7-segment displays while the remaining show the *blank* character. The letters of the word will be determined by three 2-bit wide inputs as in part 5). Furthermore the possibility to rotate the word from right-to-left should be implemented, as given in the table below.

$SW[9]$	$SW[8]$	$SW[7]$	$HEX5$	$HEX4$	$HEX3$	$HEX2$	$HEX1$	$HEX0$
0	0	0				d	E	1
0	0	1			d	E	1	
0	1	0		d	E	1		
0	1	1	d	E	1			
1	0	0	E	1				d
1	0	1	1				d	E

For the realization a VHDL entity named **e\_2bit6to1mux** must be written, which describes a 2-bit wide 6-to-1 multiplexer.

- i) Determine the truth table for this 6-to-1 multiplexer and derive the logic functions.

In total six instances of **e\_2bit6to1mux** and **e\_7segdec** will be needed, which have to be declared as **component** in the top-level entity and instantiated. Perform the following steps:

- ii) Generate a new Quartus project for the circuit named **e\_my\_rotword**.
- iii) Create a VHDL top-level entity for the circuit. Connect the switches  $SW[9 - 7]$  with the address inputs of the six instances of the 2-bit wide 6-to-1 multiplexer. Furthermore connect the switches  $SW[5 - 0]$  with the inputs of the six 7-segment decoder in a way to achieve the desired functionality. Show the position of the switches on the LEDs and connect the outputs of the six instances of the 7-segment decoder with the 7-segment displays  $HEX5$  to  $HEX0$ .
- iv) Import the necessary pin assignments.
- v) Compile the project, download the compiled circuit and test the functionality.

Furthermore inspect the circuit with **RTL Viewer** and **Chip Planner**.